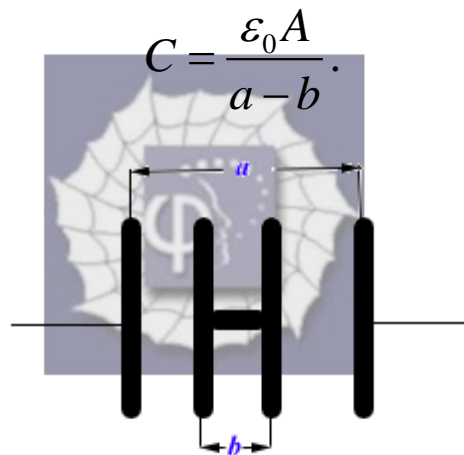


364.

**Problem 31.21 (RHK)**

*In the figure two capacitors in series have been shown. The rigid centre section of length  $b$  is movable horizontally. We have to show that the equivalent capacitance of the series combination is independent of the position of the central section and is given by*




**Solution:**

For the configuration of the capacitor plates let the separation between the plates be  $x$  and  $(a - b - x)$ .

Electric field between the plates is

$$E = \frac{q}{\epsilon_0 A}.$$

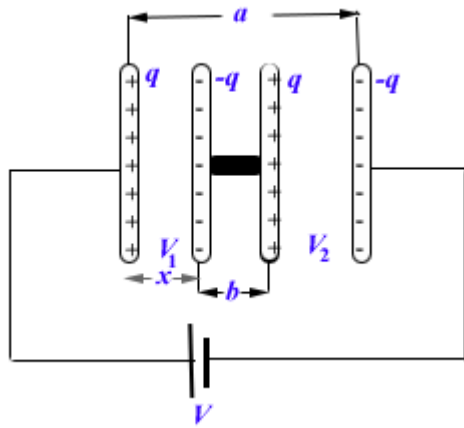

Therefore, potential differences between the pairs of plates are

$$V_1 = \frac{qx}{\epsilon_0 A},$$

and

$$V_2 = \frac{q(a-b-x)}{\epsilon_0 A}.$$

But as

$$V_1 + V_2 = V,$$

we have

$$V = \frac{qx}{\epsilon_0 A} + \frac{q(a-b-x)}{\epsilon_0 A} = \frac{q(a-b)}{\epsilon_0 A}.$$

And

$$q = \frac{\epsilon_0 A}{(a-b)} V.$$

As

$$q = CV,$$

$$C = \frac{\epsilon_0 A}{a-b}.$$