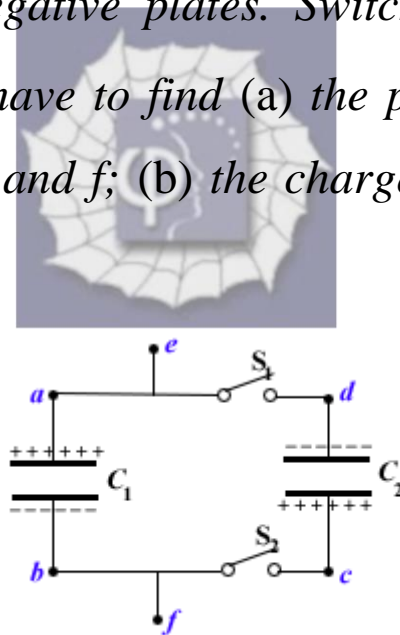


365.

Problem 31.23 (RHK)

In the figure two capacitors $C_1 = 1.16 \mu\text{F}$ and $C_2 = 3.22 \mu\text{F}$ have been shown. Each is charged to a potential $V = 96.6 \text{ V}$ but with opposite polarity, so that points a and c are on the side of the respective positive plates of C_1 and C_2 , and points b and d are on the side of the respective negative plates. Switches S_1 and S_2 are now closed. We have to find (a) the potential difference between points e and f ; (b) the charge on C_1 and (c) the charge on C_2 .



Solution:

(a)

In the circuit shown in the figure the capacitors

$C_1 = 1.16 \mu\text{F}$ and $C_2 = 3.22 \mu\text{F}$ each have been charged to potential $V = 96.6 \text{ V}$ and the switches S_1 and S_2 are open.

Therefore, the magnitude of the charge on C_1 will be

$$q_1 = 1.16 \times 10^{-6} \times 96.6 \text{ C} = 112.0 \times 10^{-6} \text{ C} = 112.0 \mu\text{C}.,$$

and the magnitude of the charge on C_2 will be

$$q_2 = 3.22 \times 10^{-6} \times 96.6 \text{ C} = 311.0 \times 10^{-6} \text{ C} = 311.0 \mu\text{C}.$$

After the switches S_1 and S_2 are closed an amount of charge $q \mu\text{C}$ will flow from C_2 to C_1 till both the capacitors have the same potential across their plates. That is the potential difference between points e and f will be the potential difference across each of the two capacitors.

This implies that

$$\frac{(311.0 - q)}{3.22 \times 10^{-6}} = \frac{(q - 112.0)}{1.16 \times 10^{-6}}.$$

Solving this equation, we find

$$q = 164.75 \mu\text{C}.$$

We calculate the potential difference across the capacitor C_1 . It will also be equal to the potential difference

between e and f after the two switches have been closed.

We have

$$V' = \frac{(164.7 - 112.0)}{1.16} \text{ V} = 45.4 \text{ V}.$$

(b)

Charge on C_1 will be

$$q_1' = (164.7 - 112.0) \mu\text{C} = 52.7 \mu\text{C},$$

(c)

And charge on C_2 will be

$$q_2' = (311 - 164.7) \mu\text{C} = 146.3 \mu\text{C}.$$

