

390.

Problem 32.31 (RHK)

An electrical cable consists of 125 strands of fine wire, each having $2.65\text{--}\mu\Omega$ resistance. The same potential difference is applied between the ends of each strand and results in a total current of 750 mA. (a) We have to find the current in each strand; (b) the applied potential difference; and (c) the resistance of the cable.

Solution:



(a)

The given electrical cable consists of 125 strands of wire.

Resistance, r , of each strand is

$$r = 2.65\ \mu\Omega = 2.65 \times 10^{-6}\ \Omega.$$

The total current flowing through the cable is

$$I = 750\ \text{mA} = 750 \times 10^{-3}\ \text{A}.$$

Therefore, current flowing in each strand of wire will be

$$i = \frac{750}{125}\ \text{mA} = 6.0\ \text{mA}.$$

(b)

As the resistance of each strand of wire is

$r = 2.65 \mu\Omega = 2.65 \times 10^{-6} \Omega$, the potential difference across each strand will be

$$V = ir = 6 \times 10^{-3} \times 2.65 \times 10^{-6} \text{ V} = 15.9 \times 10^{-9} \text{ V} = 15.9 \text{ nV}.$$

(c)

The resistance of the cable will be

$$R = \frac{V}{I} = \frac{15.9 \times 10^{-9}}{750 \times 10^{-3}} = 21.2 \times 10^{-9} \Omega = 21.2 \text{ n}\Omega.$$

