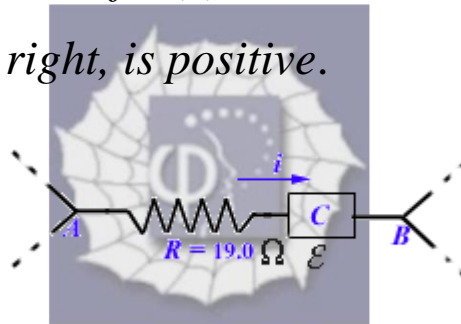


404.

Problem 33.9 (RHK)

A section of the circuit AB (see figure) absorbs 53 W of power when a current $i = 1.20$ A passes through it in the indicated direction. (a) We have to find the potential difference between A and B. (b) Assuming that the element C does not have any internal resistance, we have to find the emf. (c) We have to answer which terminal, left or right, is positive.



Solution:

(a)

The section of the circuit AB shown in the figure absorbs 53.0 W of power when a current $i = 1.20$ A passes through it. We have to find the potential difference between A and B.

Joule heat in the resistance $R = 19 \Omega$ will be

$$P_1 = i^2 R = 1.20^2 \times 19 \text{ W} = 27.36 \text{ W}.$$

Therefore, the power absorbed in the element C will be

$$P_2 = P - P_1 = (53.0 - 27.36) \text{ W} = 25.60 \text{ W}.$$

(b) and (c)

As the device *C* is without internal resistance, it has to be a source of emf. The energy that is being absorbed by *C* is getting converted into chemical energy through the charging process. Therefore, the left terminal of *C* will be positive. The emf of *C* can be found from the relation

$$P_2 = E_i,$$

and

$$E = \frac{P_2}{i} = \frac{25.60}{1.20} \text{ V} = 21.37 \text{ V}.$$

The potential difference *A* and *B* will, therefore, be $-19.0 \times 1.2 (\Omega \text{ A}) - 21.37 \text{ V} = -44.17 \text{ V}.$

That is *B* is at -44.17 V , if *A* is at 0.0 V .