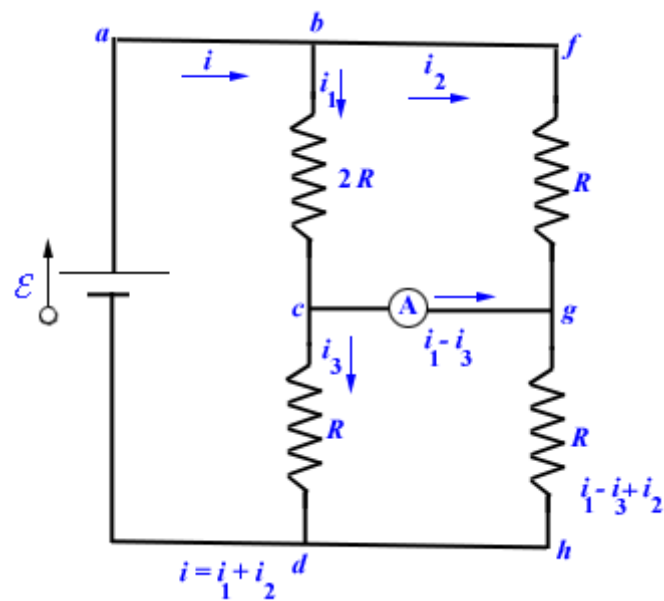


411.

Problem 33.33 (RHK)

In the circuit shown in the figure, we have to find the current flowing through the ammeter A , assuming that A has zero resistance.



Solution:

It is a multi-loop circuit. We have indicated currents in different branches of the circuit by taking care of conservation of charge. We have three unknown currents, i , i_1 and i_3 , as $i_2 = i - i_1$.

Considering the circuit $abcde$ and applying Kirchoff's law, we get

$$-2Ri_1 - i_3R + E = 0,$$

or

$$2Ri_1 + i_3R = E.$$

Applying Kirchoff's law to loops *bfgc* and *cghd*, we get

$$-(i - i_1)R + 2Ri_1 = 0, \text{ or } i_1 = \frac{i}{3},$$

and

$$-(i - i_3)R + i_3R = 0, \text{ or } i_3 = \frac{i}{2}.$$

We now have three linear equations connecting i_1 , i_3 and i . We solve them and find

$$i = \frac{6E}{7R}, \quad i_1 = \frac{2E}{7R}, \quad \text{and } i_3 = \frac{3E}{7R}.$$

Therefore, the current in the ammeter, $|i_1 - i_3|$, will be

$$\frac{3E}{7R} - \frac{2E}{7R} = \frac{E}{7R}.$$