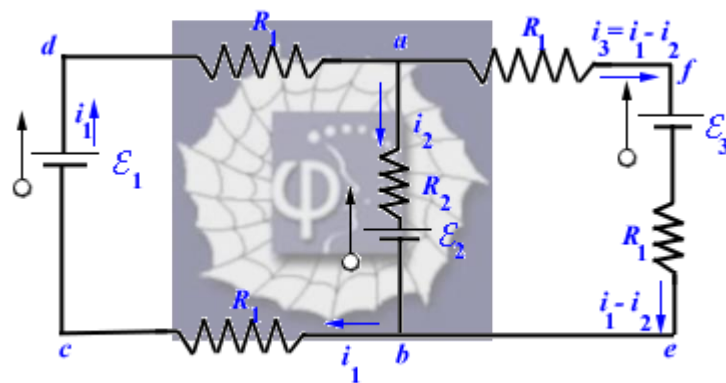


413.

**Problem 33.37 (RHK)**

We have to calculate (a) the current through each source of emf in the circuit shown in the figure. (b) We have to calculate  $V_b - V_a$ . We may assume that  $R_1 = 1.20 \Omega$ ,  $R_2 = 2.30 \Omega$ ,  $E_1 = 2.00 \text{ V}$ ,  $E_2 = 3.80 \text{ V}$ , and  $E_3 = 5.00 \text{ V}$ .



**Solution:**

In the circuit shown above currents have been indicated in the different branches, and its multi-loops can be fixed by affixing labels to corners and intersections.

Data of the problem are

$R_1 = 1.20 \Omega$ ,  $R_2 = 2.30 \Omega$ ,  $E_1 = 2.00 \text{ V}$ ,  $E_2 = 3.80 \text{ V}$   
and  $E_3 = 5.00 \text{ V}$ .

(b)

We will solve this problem by applying Kirchoff's laws to different loops in the circuit.

Applying Kirchoff's laws to loops *dabcd* and *afeba*, we write the following two equations:

$$-i_1 R_1 - i_2 R_2 - E_2 - i_1 R_1 + E_1 = 0,$$

or

$$2i_1 R_1 + i_2 R_2 = E_1 - E_2. \quad (\text{A})$$

and

$$-(i_1 - i_2) R_1 - E_3 - (i_1 - i_2) R_1 + E_2 + i_2 R_2 = 0$$

or

$$-2i_1 R_1 + 2i_2 R_1 + i_2 R_2 = E_3 - E_2. \quad (\text{B})$$

Solving equations (A) and (B), we find

$$i_2 = \frac{E_1 + E_3 - 2E_2}{2(R_1 + R_2)},$$

and

$$i_1 = \frac{(R_2 + 2R_1)E_1 - 2R_1E_2 - R_2E_3}{4R_1(R_1 + R_2)}.$$

Substituting the data given above, we find

$$i_2 = -85.7 \text{ mA},$$

and

$$i_1 = -668 \text{ mA}.$$

The current flowing through  $E_3$  is

$$i_1 - i_2 = -582.3 \text{ mA.}$$

As we are interested in the magnitudes of currents and not their directions, the currents flowing through  $E_1$ ,  $E_2$  and  $E_3$  are 668 mA, 85.7 mA and 582.3 mA, respectively.

(a)

From the section  $ba$  of the circuit, we calculate  $V_a - V_b$ .

We have

$$\begin{aligned} V_a - V_b &= E_2 + i_2 R_2 = (3.80 - 85.7 \times 2.3 \times 10^{-3}) \text{ V} \\ &= 3.60 \text{ V.} \end{aligned}$$

