415.

Problem 33.40 (RHK)

A simple ohmmeter is made by connecting a 1.50-V flashlight battery in series with a resistor R and a 1.00mA ammeter, as shown in the figure. R is adjusted so that when the circuit elements are shorted together the meter deflects its full-scale value of 1.00 mA. We have to calculate the values of the resistances across the terminal which would give a deflection of (a) 10%, (b) 50%, and (c) 90% of full scale. (d) If the ammeter has a resistance of 18.5 Ω and the internal resistance of the battery is negligible, we have to calculate the value of R.



Solution:

In the figure circuit diagram of an ohmmeter has been drawn. When the clip leads are shorted together, it is given that the 1.0-mA ammeter shows full scale deflection. That is a 1.0 mA current is flowing through the circuit. Assuming that the ammeter and the battery have negligible resistances, the value of the resistance *R* will have to be

$$R = \frac{1.5 \text{ V}}{1.0 \times 10^{-3} \text{ A}} = 1500 \text{ }\Omega.$$
(b)

If the ammeter shows 10% deflection of the full scale, the current in the circuit will be 0.1 mA. Therefore, the external resistance, R_x , across the leads will be as given

by the relation

$$R_x + 1500 \ \Omega = \frac{1.5 \text{ V}}{0.1 \times 10^{-3} \text{ A}} = 15000 \ \Omega,$$
or
 $R_x = 13,500 \ \Omega = 13.5 \text{ k}\Omega.$
(c)

If the ammeter shows a 50% deflection of the full scale, the current in the circuit will be 0.5 mA. The resistance, R_x , will be given by the relation

$$R_{x} + 1500 \ \Omega = \frac{1.5 \text{ V}}{0.5 \times 10^{-3} \text{ A}} = 3000 \ \Omega,$$

or
$$R_{x} = 1500 \ \Omega = 1.5 \text{ k}\Omega.$$

(d)

If the ammeter shows a 90% deflection of the full scale, the current in the circuit will be 0.9 mA. The resistance, R_x , will be given by the relation

$$R_x + 1500 \ \Omega = \frac{1.5 \text{ V}}{0.9 \times 10^{-3} \text{ A}} = 1666 \ \Omega,$$

or

$$R_x = 166.6 \ \Omega.$$

(e)

If the ammeter has a resistance of 18.5 Ω and the internal resistance of the battery is negligible, the required value of *R* will be given by the equation

$$R + 18.5 \ \Omega = \frac{1.5 \ V}{1.0 \times 10^{-3} \ A} = 1500 \ \Omega,$$

or
$$R = 1481.5 \ \Omega.$$