


418.

Problem 33.43 (RHK)

A voltmeter resistance R_V and an ammeter resistance R_A are connected to measure a resistance R , using a circuit as shown in the figure. The resistance is given by $R = V/i$, where V is the voltmeter reading and i is the current in the resistor R . Some of the current registered by the ammeter (i') goes through the voltmeter so that the ratio of the meter readings ($= V/i'$) gives only an apparent resistance reading R' . We have to show that R and R' are related by

$$\frac{1}{R} = \frac{1}{R'} - \frac{1}{R_V}.$$

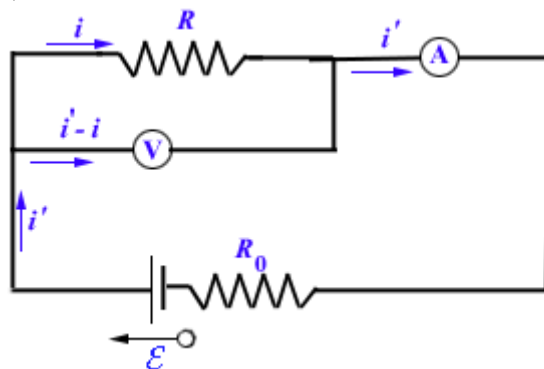Note that as $R_V \rightarrow \infty$, $R' \rightarrow R$.



Solution:

Let the resistance of the voltmeter be R_v . As the voltmeter is connected in parallel with the resistance R , currents $i' - i$ flowing through the voltmeter and i flowing through the resistance R are related as

$$(i' - i)R_v = iR,$$

or

$$i(R + R_v) = i'R_v.$$

The measured resistance

$$R' = \frac{V}{i'}.$$

Therefore, we have

$$\frac{i(R + R_v)}{V} = \frac{i'R_v}{V},$$

or

$$\frac{(R + R_v)}{R} = \frac{R_v}{R'},$$

or

$$\frac{1}{R} = \frac{1}{R'} - \frac{1}{R_v}.$$

We note that as $R_v \rightarrow \infty$, $R' \rightarrow R$.

