

421.

Problem 33.52 (RHK)

A controller on an electronic arcade game consists of a variable resistor connected across the plates of a 220-nF capacitor. The capacitor is charged to 5.00 V, then discharged through the resistor. The time for the potential difference to decrease to 800 mV is measured by an internal clock. We have to find the range of the resistance of the resistor, if the range of discharge times that can be handled is from 10.0 μs to 6.0 ms.



Solution:

Capacitance of the capacitor is

$$C = 220 \times 10^{-9} \text{ F.}$$

As equation for discharge of a capacitor in a RC circuit is

$$q(t) = q_0 e^{-t/RC}.$$

Therefore, variation of voltage across the capacitor as it discharges with time will be given by the equation

$$V(t) = V_0 e^{-t/RC}.$$

It is given that an internal clock measures time, t , for the voltage of the capacitor charged to 5.00 V to drop to 800 mV. Therefore, relation between t and the resistance R is

$$-\frac{t}{RC} = \ln\left(\frac{800 \times 10^{-3}}{5}\right)$$

$$= \ln(0.16) = -1.8326,$$

or

$$t = 1.8326 \times 220 \times 10^{-9} R \left(\Omega^{-1}\text{s}\right) = 4.03 \times 10^{-7} R \left(\Omega^{-1}\text{s}\right).$$

And

$$R = \frac{t(\text{s})}{4.03 \times 10^{-7}} \left(\Omega\right).$$

(a)

For $t = 10.0 \mu\text{s} = 1.0 \times 10^{-5} \text{ s}$,

resistance in the circuit has to be

$$R = \frac{10^{-5}}{4.03 \times 10^{-7}} \left(\Omega\right) = 24.8 \Omega.$$

(b)

For $t = 6.0 \text{ ms} = 6.0 \times 10^{-3} \text{ s}$,

resistance in the circuit has to be

$$R = \frac{6 \times 10^{-3}}{4.03 \times 10^{-7}} \left(\Omega\right) = 14,888.0 \Omega = 14.88 \text{ k}\Omega.$$

Therefore, the range of the resistance of the resistor has to be from 24.8Ω to $14.9 \text{ k}\Omega$.

