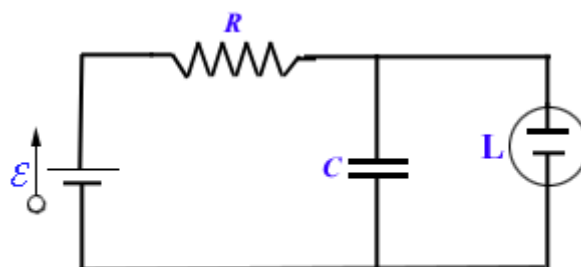


422.

**Problem 33.53 (RHK)**

*In the figure a circuit has been shown of a flashing lamp of the type that is attached to barrels at highway construction sites. The fluorescent lamp **L** is connected in parallel across the capacitor **C** of an RC circuit. Current passes through the lamp only when the potential across it reaches the breakdown voltage  $V_L$ ; in this event the capacitor discharges through the lamp and it flashes for a very short time. Suppose that two flashes per second are needed. We have to calculate the resistance **R** of the resistor for a lamp with breakdown voltage  $V_L = 72 \text{ V}$  which is used with a 95-V battery, and a  $0.15\text{-}\mu\text{F}$  capacitor.*



**Solution:**

In the figure circuit has been drawn of a flashing lamp.

Capacitance of the capacitor in the circuit is

$$C = 0.15 \mu\text{F} = 0.15 \times 10^{-6} \text{ F.}$$

EMF of the battery is

$$E = 95.0 \text{ V.}$$

The breakdown voltage of the fluorescent lamp is

$$V_L = 72.0 \text{ V.}$$

If two flashes per second are needed, the time for charging the  $0.15\text{-}\mu\text{F}$  capacitor to  $72 \text{ V}$  using  $95.0\text{-V}$  battery has to be  $0.5 \text{ s}$ . This requirement fixes the value of the resistance  $R$  in the circuit.

Equation for charging a capacitor of capacitance  $C$  in a  $RC$  circuit is

$$\frac{q(t)}{C} = \frac{q_0}{C} \left( 1 - e^{-t/RC} \right),$$

or

$$V(t) = V_0 \left( 1 - e^{-t/RC} \right).$$

In our problem

$$V_0 = 95.0 \text{ V.}$$

If the lamp has to flash in  $t = 0.5 \text{ s}$ , voltage across the capacitor has to build from  $V = 0 \text{ V}$  to  $V = V_L = 72.0 \text{ V}$  in  $0.5 \text{ s}$ . This requirement will determine the resistance  $R$ .

Therefore,

$$\frac{V_L}{V_0} - 1 = -e^{-0.5/RC},$$

or

$$\frac{72}{95} - 1 = -e^{-0.5/RC},$$

or

$$\frac{23}{95} = e^{-0.5/RC},$$

or

$$R = \frac{(-0.5)}{C \times \ln\left(\frac{23}{95}\right)} \Omega = \frac{0.5}{0.15 \times 10^{-6} \times 1.4184} \Omega = 2.35 \text{ M}\Omega.$$

