

423.

Problem 33.58 (RHK)

An initially uncharged capacitor C is fully charged by a constant emf E in series with a capacitor R . (a) We have to show that the final energy stored in the capacitor is half the energy supplied by the emf. (b) By direct integration of i^2R over the charging time, we have to show that the internal energy dissipated by the resistor is also half the energy supplied by the emf.



Solution:

(a)

The charging equation for a capacitor of capacitance C connected with a resistor or resistance R to a source of emf E is

$$q(t) = q_0 \left(1 - e^{-t/RC} \right),$$

where

$$q_0 = CE.$$

By differentiating $q(t)$ with respect to the variable t , we will obtain the current as a function of time, $i(t)$, during the charging process. That is

$$i(t) = \frac{dq(t)}{dt} = -q_0 \left(-\frac{1}{RC} \right) e^{-t/RC} = \frac{q_0}{RC} e^{-t/RC} = \frac{E}{R} e^{-t/RC}.$$

The energy supplied by the emf in charging the capacitor fully will be given by the integral

$$U = \int_0^{\infty} E i(t) dt = \int_0^{\infty} \frac{E^2}{R} e^{-t/RC} dt = \frac{E^2}{R} (-RC) \left[e^{-t/RC} \right]_0^{\infty} = CE^2.$$

The final energy stored in the capacitor is

$$U_c = \frac{q_0^2}{2C} = \frac{(CE)^2}{2C} = \frac{CE^2}{2}.$$

Therefore, it is half the energy supplied by the source of emf.

(b)

We next calculate the internal energy dissipated in the resistor.

Joule heat per second is

$$P(t) = i^2(t)R.$$

Therefore, the total energy dissipated in the resistor during the charging process will be given by integrating $P(t)$ over the charging time. That is

$$\begin{aligned}
 U_R &= \int_0^{\infty} P(t) dt = \int_0^{\infty} i^2(t) R dt = \int_0^{\infty} \frac{E^2}{R^2} e^{-2t/RC} R dt \\
 &= \frac{E^2}{R} \int_0^{\infty} e^{-2t/RC} dt \\
 &= \frac{E^2}{R} \left(-\frac{RC}{2} \right) \left[e^{-2t/RC} \right]_0^{\infty} \\
 &= \frac{E^2 C}{2}.
 \end{aligned}$$

This is also equal to half the energy supplied by the emf in charging the capacitor.

