

424.

**Problem 33.55 (RHK)**

A  $3.0\text{-M}\Omega$  resistor and a  $1.0\text{-}\mu\text{F}$  capacitor are connected in a single loop circuit with a seat of emf with  $E = 4.0\text{ V}$ . At  $1.0\text{ s}$  after the connection is made, we have to find the rates at which (a) the charge on the capacitor is increasing, (b) the energy is being stored in the capacitor, (c) internal energy is appearing in the resistor, and (d) the energy is being delivered by the seat of emf.



**Solution:**

The variation of charge on a capacitor with time during the charging process is given by the equation

$$q(t) = q_0 \left( 1 - e^{-t/RC} \right),$$

where,  $q_0 = EC$ .

The rate of change of charge,  $\frac{dq(t)}{dt}$ , is the current  $i(t)$ .

It is

$$i(t) = \frac{dq(t)}{dt} = \frac{q_0}{RC} e^{-t/RC}. \quad (\text{A})$$

The internal energy in the capacitor at time,  $t$ , will be

$$U_C(t) = \frac{q^2(t)}{2C}.$$

Therefore,

$$\frac{dU_C(t)}{dt} = \frac{q(t)}{C} \times \frac{dq(t)}{dt} = \frac{q_0}{C} \left(1 - e^{-t/RC}\right) \times \frac{q_0}{RC} e^{-t/RC}. \quad (\text{B})$$

The rate at which internal energy is appearing in the resistor is

$$P_R(t) = i^2(t)R = \left(\frac{q_0 e^{-t/RC}}{RC}\right)^2 \times R = \frac{q_0^2}{RC^2} e^{-2t/RC}. \quad (\text{C})$$

The rate at which the energy is being delivered by the seat of emf is

$$P_B(t) = Ei(t) = \frac{Eq_0}{RC} e^{-t/RC}. \quad (\text{D})$$

Data of our problem are:

$$R = 3.0 \times 10^6 \, \Omega,$$

$$C = 1.0 \times 10^{-6} \, \text{F},$$

$$\therefore RC = 3 \, \text{s},$$

$$q_0 = EC = 4.0 \times 10^{-6} \, \text{C}.$$

In equations (A), (B), (C) and (D), we will substitute the above values and use  $t = 1.0 \, \text{s}$ . We find

(a)

The rate of change of charge at  $t = 1.0$  s is

$$\frac{dq(t = 1.0 \text{ s})}{dt} = \frac{4.0 \times 10^{-6}}{3} e^{-1/3} = 0.955 \mu\text{C s}^{-1},$$

as

$$e^{-1/3} = 0.7165.$$

(b)

The rate at which the energy is being stored in the capacitor is at  $t = 1.0$  s is

$$\begin{aligned} \frac{dU_C(t = 1.0 \text{ s})}{dt} &= \frac{E^2}{R} (1 - e^{-1/3}) e^{-1/3} \\ &= \frac{16}{3.0 \times 10^6} (1 - e^{-1/3}) e^{-1/3} \text{ J s}^{-1} \\ &= 1.08 \mu\text{W}. \end{aligned}$$

(c)

The rate at which internal energy is appearing in the resistor at  $t = 1.0$  s is

$$\begin{aligned} P_R(t = 1.0 \text{ s}) &= \frac{q_0^2}{RC^2} e^{-2/3} = \frac{E^2}{R} e^{-2/3} = \frac{16}{3 \times 10^6} e^{-2/3} \text{ W} \\ &= 2.74 \mu\text{W}. \end{aligned}$$

(d)

The rate at which the energy is being delivered by the seat of emf at  $t = 1.0$  s is

$$P_B(t = 1.0 \text{ s}) = \frac{Eq_0}{RC} e^{-1/3} = \frac{E^2}{R} e^{-1/3} = \frac{16}{3 \times 10^6} e^{-1/3} \text{ W} \\ = 3.82 \mu\text{W}.$$

