

530.

**Problem 38.67 (RHK)**

*We have to find the resistance  $R$  that should be connected to an inductor  $L=220$  mH and capacitor  $C=12$   $\mu$ F in series in order that the maximum charge on the capacitor decays to 99% of its initial value in 50 cycles.*

**Solution:**

In a LCR circuit the variation of charge as a function of time is given by the function

$$q = q_m e^{-Rt/2L} \cos(\omega't + \phi),$$

in which

$$\omega' = \sqrt{\omega^2 - (R/2L)^2}.$$

The inductance in the circuit is

$$L = 220 \text{ mH},$$

and the capacitance in the circuit is

$$C = 12 \mu\text{F}.$$

Therefore, the period of  $LC$ -oscillations will be

$$T = 2\pi\sqrt{LC} = 2\pi\sqrt{220 \times 10^{-3} \times 12 \times 10^{-6}} \text{ s} = 0.0102 \text{ s}.$$

We want to fix the resistance in the  $LCR$ -circuit in order that the maximum charge on the capacitor decays to 99% of its initial value in 50 cycles, that is in

$$t = 50 \times 0.0102 \text{ s} = 0.51 \text{ s}.$$

We have the condition

$$\frac{99}{100} = e^{-R \times 0.51 / 2 \times 220 \times 10^{-3}} = e^{-1.159R},$$

or

$$\ln(.99) = -1.159R,$$

$$\therefore R = \frac{1.005 \times 10^{-2}}{1.159} \Omega = 8.67 \text{ m}\Omega.$$

