

531.

Problem 38.71 (RHK)

We have to show that in a damped LC circuit the fraction of the energy lost per cycle of oscillation, $\Delta U/U$, is given to a close approximation by $2\pi R/\omega L$. The quantity $\omega L/R$ is often called the Q of the circuit (for “quality”). A “high- Q ” circuit has low resistance and a low fractional energy loss per cycle ($= 2\pi/Q$).



Solution:

The differential equation giving the variation of charge q as a function of time in a damped LC circuit is

$$L \frac{d^2 q}{dt^2} + R \frac{dq}{dt} + \frac{q}{C} = 0.$$

The solution of this differential equation is

$$q = q_m e^{-Rt/2L} \cos(\omega't + \phi),$$

where

$$\omega' = \sqrt{\omega^2 - (R/2L)^2}.$$

Assuming that

$$\omega = \frac{1}{\sqrt{LC}} \quad ? \quad \frac{R}{2L},$$

current can be approximated by the function

$$i = \frac{dq}{dt}; \quad -q_m \omega e^{-Rt/2L} \sin(\omega't + \phi).$$

The total electromagnetic energy at any instant in the LC circuit is the sum of electrical energy stored in the capacitor and the magnetic energy stored in the inductor.

That is

$$\begin{aligned} U &= \frac{1}{2} Li^2 + \frac{q^2}{2C} = \frac{1}{2} L \omega^2 (q_m)^2 e^{-Rt/L} \sin^2(\omega't + \phi) + \\ &\quad + \frac{1}{2C} (q_m)^2 e^{-Rt/L} \cos^2(\omega't + \phi) \\ &= \frac{1}{2} L \omega^2 (q_m)^2 e^{-Rt/L}. \end{aligned}$$

The dissipation of energy in the LC circuit in the resistor R is given by the relation

$$\frac{dU}{dt} = -i^2 R; \quad -(q_m)^2 R \omega^2 e^{-Rt/L} \sin^2(\omega't + \phi).$$

The total dissipation of energy over one cycle will therefore be given by the integral

$$\begin{aligned} \Delta U &= \int_0^{2\pi/\omega} \frac{dU}{dt} dt = q_m^2 \omega^2 R e^{-Rt/L} \times \frac{1}{2} \times \frac{2\pi}{\omega} \\ &= \pi q_m^2 \omega R e^{-Rt/L}. \end{aligned}$$

$$\therefore \frac{\Delta U}{U} = \frac{2\pi R}{L\omega}.$$

The quantity $\omega L/R$ is called the Q of the circuit.

Thus

$$\frac{\Delta U}{U} = \frac{2\pi}{Q}.$$

