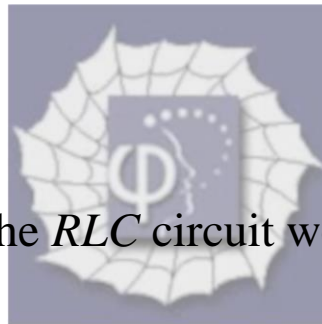


535.

Problem 39.17 (RHK)

For a certain RLC circuit the maximum generator emf is 125 V and the maximum current is 3.20 A. If the current leads the generator emf by 56.3° , (a) we have to find the impedance, (b) the resistance of the circuit. (c) We have to answer whether the circuit is predominantly capacitive or inductive.

Solution:



From the data of the *RLC* circuit we note that

$$E_m = 125 \text{ V} ,$$

and

$$i_m = 3.2 \text{ A} .$$

Therefore, the impedance of the circuit

$$Z = \frac{E_m}{i_m} = \frac{125}{3.2} \Omega = 39.06 \Omega .$$

It is given that the current leads the generator emf by

$$\phi = 56.3^\circ .$$

As

$$\cos \phi = \frac{R}{Z},$$

$$R = 39.06 \times \cos(56.3^\circ) \Omega = 21.7 \Omega.$$

As the current is leading the emf the circuit is predominantly capacitive.

