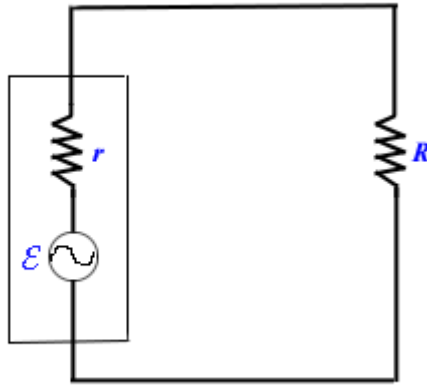


539.

Problem 39.29 (RHK)

We have to show that in the circuit shown in the figure the power dissipated in the resistance R is maximum when $R=r$, in which r is the internal resistance of the AC generator.



Solution:

Let the emf of the AC-generator be

$$E = E_m \sin \omega t .$$

As the total resistance in the resistance in the circuit is

$R + r$, the current i in the circuit will be

$$i = \left(\frac{E_m}{R + r} \right) \sin \omega t .$$

The average power dissipated in the circuit will be

$$\bar{P} = i_{rms}^2 R = \frac{1}{2} \times \left(\frac{E_m}{R+r} \right)^2 R.$$

The function $\bar{P}(R)$ will have an extremum at R for which

$$\frac{d\bar{P}}{dR} = 0.$$

This condition gives

$$\frac{1}{(R+r)^2} - \frac{2R}{(R+r)^3} = 0,$$

or

$$R+r-2R=0,$$

or

$$R=r.$$

By calculating $\left. \frac{d^2 \bar{P}(R)}{dR^2} \right|_{R=r}$, we will show that it is <0 ,

and therefore $\bar{P}(R=r)$ is a maximum.

$$\begin{aligned} \left. \frac{d^2 \bar{P}(R)}{dR^2} \right|_{R=r} &= \frac{1}{2} \mathcal{E}_m^2 \left\{ -\frac{2}{(R+r)^3} - \frac{2}{(R+r)^3} + \frac{6R}{(R+r)^4} \right\}_{R=r} \\ &= -\frac{\mathcal{E}_m^2}{16r^3} < 0. \end{aligned}$$

The power dissipation is maximum when the external load is equal to the load of the generator.

